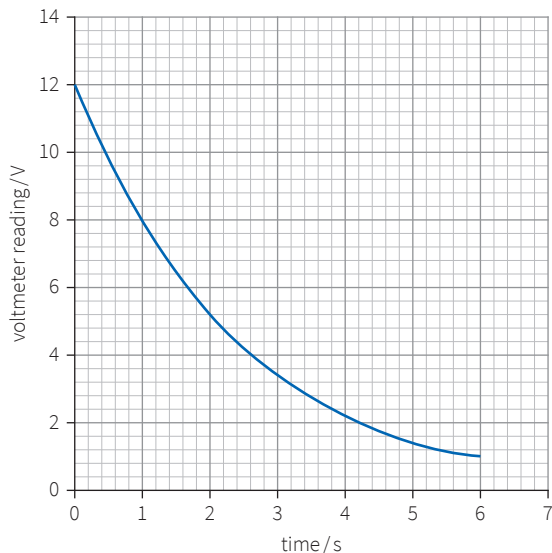


A Level AQA Physics

16 Capacitance – answers

Question	Answers	Extra information	Mark	AO	Spec reference
01.1	$Q = CV = 1000 \times 10^{-6} \times 12 = 1.2 \times 10^{-2} \text{ C}$ $I = \frac{V}{R} = \frac{12 \text{ V}}{2400 \Omega} = 5.0 \times 10^{-3} \text{ A}$		1 1	2	3.7.4.2
01.2	Time for p.d. to drop to half its value $= RC \ln 2 = 2400 \times 1000 \times 10^{-6} \times 0.693 = 1.67 \text{ s}$	Graph with scales/labelled axes extending to 6 seconds Initial p.d. = 12 V and exponential shape by eye Evidence for p.d. halving in 1.7 s	1 1 1	2	3.7.4.4
01.3	Original time constant = $RC = 2400 \times 1000 \times 10^{-6} = 2.4 \text{ s}$ New time constant = $1.8 \times 2.4 = 4.32 \text{ s}$ Effective capacitance = $\frac{4.32}{2400} = 1.8 \times 10^{-3} \text{ F}$ Capacitances in parallel add so $C_{\text{total}} = C + 1000 \times 10^{-6} \text{ F} = 1.8 \times 10^{-3} \text{ F}$ $C = 0.8 \times 10^{-3} \text{ F} = 800 \mu\text{F}$	Calculation of new time constant/ method involving time constant Answer	1 1 1	3	3.7.4.4



A Level AQA Physics

16 Capacitance – answers

Question	Answers	Extra information	Mark	AO	Spec reference
01.4	Assumption is that the voltmeter has infinite resistance If the voltmeter has a large but finite resistance, this reduces the resistance of the circuit because there are now two resistances in parallel The time constant will be smaller than it should be, so the unknown capacitance is larger than the value in 06.3	Effect of resistance of voltmeter on resistance of circuit	1	1	3.7.4.4
		Effect on capacitance	1	3	
02.1	From the graph, the time for the pd to halve 0.12 ms Time to halve = $RC \ln 2$ Time constant = $RC = \frac{(\text{time to halve})}{0.693} = 1.73 \times 10^{-4} \text{ s}$	Use of graph to find time to halve	1	2	3.7.4.4
		Answer	1		
02.2	$C = \frac{\text{time constant}}{R}$ $= \frac{2.89 \times 10^{-4}}{10 \times 10^3}$ $= 2.89 \times 10^{-8} \text{ F}$	Use of time constant to find C	1	2	3.7.4.4
			1		
02.3	Curve that starts at half the pd on the y-axis, and has $T_{1/2}$ that is double the original value by eye If the resistance doubles, the maximum current will halve, so the maximum pd will halve If the resistance is doubled, the time constant is doubled, so the time to halve the p.d. is also doubled	Correct line on graph	1	3	3.7.4.4
		Explanation of p.d. $\times \frac{1}{2}$	1		
		Explanation of time to halve $\times 2$	1		
02.4	Use the pd and resistance to work out the current using $I = \frac{V}{R}$ The area under the graph is the charge stored; work out the charge represented by each square using $Q = It$; count squares and multiply	Conversion of pd to current	1	3	3.7.4.4
		How to find charge from area	1		

A Level AQA Physics

16 Capacitance – answers

Question	Answers	Extra information	Mark	AO	Spec reference																																
03.1	<p>When the switch is closed, there is a potential difference across the resistor A current flows, so the charge on the capacitor decreases</p> <p>As the charge decreases, the p.d. decreases ($V = \frac{Q}{C}$), so the current decreases in the same way</p> <p>The rate of change of pd depends on the charge, and hence pd, so the relationship is a negative exponential</p>	<p>Link between p.d. and current</p> <p>Link to charge on capacitor</p> <p>Explanation of exponential</p>	1 1 1	1	3.7.4.2																																
03.2	<table border="1"> <thead> <tr> <th>Time / min</th> <th>p.d. / V</th> <th>Time / s</th> <th>ln V</th> </tr> </thead> <tbody> <tr> <td>0</td> <td>2.50</td> <td>0</td> <td>0.92</td> </tr> <tr> <td>10</td> <td>1.62</td> <td>600</td> <td>0.482426</td> </tr> <tr> <td>20</td> <td>1.08</td> <td>1200</td> <td>0.076961</td> </tr> <tr> <td>30</td> <td>0.70</td> <td>1800</td> <td>-0.35667</td> </tr> <tr> <td>40</td> <td>0.46</td> <td>2400</td> <td>-0.77653</td> </tr> <tr> <td>50</td> <td>0.30</td> <td>3000</td> <td>-1.20397</td> </tr> <tr> <td>60</td> <td>0.20</td> <td>3600</td> <td>-1.60944</td> </tr> </tbody> </table> 	Time / min	p.d. / V	Time / s	ln V	0	2.50	0	0.92	10	1.62	600	0.482426	20	1.08	1200	0.076961	30	0.70	1800	-0.35667	40	0.46	2400	-0.77653	50	0.30	3000	-1.20397	60	0.20	3600	-1.60944	<p>Calculations of t in seconds and $\ln V$</p> <p>do not penalise excessive significant figures.</p> <p>Graph starting at (0, 0), points plotted, linear line of best fit</p> <p>Correct labels/units</p>	1 1 1	2	3.7.4.4
Time / min	p.d. / V	Time / s	ln V																																		
0	2.50	0	0.92																																		
10	1.62	600	0.482426																																		
20	1.08	1200	0.076961																																		
30	0.70	1800	-0.35667																																		
40	0.46	2400	-0.77653																																		
50	0.30	3000	-1.20397																																		
60	0.20	3600	-1.60944																																		


A Level AQA Physics

16 Capacitance – answers

Question	Answers	Extra information	Mark	AO	Spec reference
03.3	$V = V_0 e^{-\frac{t}{RC}}$ $\ln V = \ln V_0 - \frac{t}{RC}$ So a graph of $\ln V$ against t gradient = $-\frac{1}{RC}$	Taking natural logs of both sides of equation Gradient correct	1 1	2	3.7.4.4
03.4	$\ln(1.5) = 0.405$ Reading from graph when $\ln V = 0.4$, $t = 700$ s = 11 minutes and 40s	Correct deduction from graph	1	2	3.7.4.4
04.1	$E = \frac{1}{2} CV^2$ $= \frac{1}{2} \times 470 \times 10^{-6} \times (6.0)^2$ $= 8.46 \times 10^{-3} \text{ J} = 8.5 \times 10^{-3} \text{ J}$	Answer	1	2	3.7.4.3
04.2	Resistance of lamp = $\frac{6.0}{0.3} = 20 \Omega$ Time to discharge to 37% = $RC = 470 \times 10^{-6} \times 20 = 9.4 \times 10^{-3} \text{ s}$ energy transferred = $8.46 \times 10^{-3} \times 0.37^2 = 1.158 \times 10^{-3} \text{ J}$ power = $\frac{\text{energy}}{\text{time}} = \frac{1.158 \times 10^{-3}}{9.4 \times 10^{-3}} = 0.12 \text{ W}$ You may not see this as it is less than a tenth of the bulbs normal power rating power = $6 \text{ V} \times 0.3 \text{ A} = 1.8 \text{ W}$	Calculation of resistance Explicit use of RC as time for pd to reduce to 37% energy transferred from capacitor $\propto V^2$ Calculation of power Appropriate comment with numerical comparison	1 1 1 1	3	3.7.4.3
04.3	The energy stored would be multiplied by 4 as energy stored depends on V^2 The time is the same Power would be multiplied by 4; this would definitely be observable but still dim	Reference to E proportional to V^2 Effect on what is observed / appropriate comment	1 1	3	3.7.4.3

A Level AQA Physics

16 Capacitance – answers

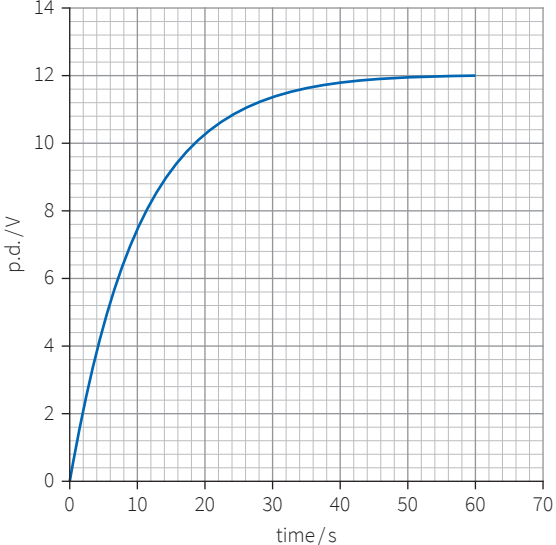Question	Answers	Extra information	Mark	AO	Spec reference
04.4	<p>(use of $E = \frac{1}{2}CV^2$)</p> <p>a 470 μF capacitor would need a pd of $V = \sqrt{\frac{2E}{C}} = 650 \text{ V}$</p> <p>a 6 V p.d. would need a capacitance of $C = \frac{E}{2V^2} = 1.4 \text{ F}$</p> <p>1.4 F is a very large capacitor, so the energy stored is achieved by increasing the p.d.</p>	<p>Comment on size of capacitance</p>	<p>1</p> <p>1</p> <p>1</p>	3	3.7.4.3
05.1	 <p>Initially there is no charge on the capacitor, so zero pd; as the capacitor charges the p.d. increases as $V = \frac{Q}{C}$</p> <p>And increases at a decreasing rate</p>	<p>Exponential growth by eye Asymptotic to 12 V</p> <p>Only a sketch needed, so no values needed on x-axis</p> <p>Correct description of V proportional to charge Comment about shape</p>	<p>1</p> <p>1</p> <p>1</p>	1	3.7.4.4


A Level AQA Physics

16 Capacitance – answers

Question	Answers	Extra information	Mark	AO	Spec reference
05.2	Reducing the resistance; as the current normally decreases as the capacitor charges, a smaller resistance is needed to maintain the current at a constant value	Answer and reason needed for mark	1	3	3.7.4.4
	The graph will be a straight line through (0, 0) as the pd increases at a constant rate		1		
	The graph will be horizontal when the capacitor is fully charged		1		
05.3	Procedure described, for example:	Sufficient detail		1	3.7.4.4
	• note the capacitance of the capacitor	Using the graph to find the time	1		
	• open the switch and short circuit the capacitor to ensure that it is uncharged	Calculating charge from current and time	1		
	• close the switch and reduce the resistance of the variable resistor to maintain the current at a constant value	Repetition/finding mean	1		
05.4	• when the graph on the computer is horizontal, open the switch			1	3.7.4.4
	• use the graph to find the time it took to charge the capacitor from time the pd started to rise until the time the pd was constant				
06.1	• multiply the current by the time to work out the charge			2	3.7.4.2
	• replace the capacitor with one of a different capacitance, and repeat				
06.1	• repeat for a range of capacitors			1	3.7.4.2
	• repeat the experiment three times for each capacitor, and calculate the mean charge stored				
06.1	• plot a graph of charge against capacitance			1	3.7.4.2
	Appropriate suggestion and solution, for example: The reading on the ammeter will not be constant as it will be difficult to change the resistance to exactly match the exponential decay of current Repeating the experiment many more times will give a more accurate measurement				

A Level AQA Physics

16 Capacitance – answers

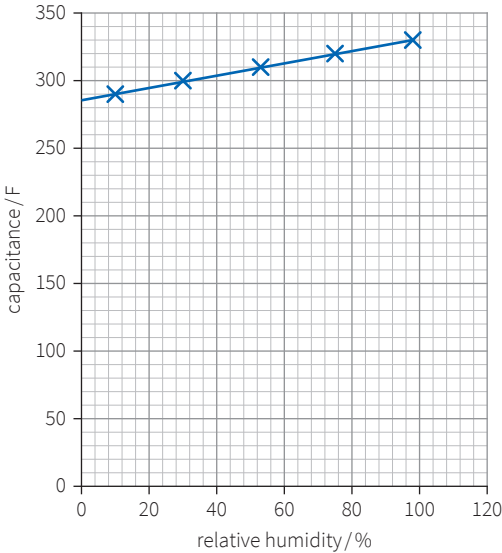Question	Answers	Extra information	Mark	AO	Spec reference
06.2	<p>The greater the humidity, the greater the capacitance The water molecules effectively reduce the distance between the plates of the capacitor, and $C = \frac{A\epsilon_0\epsilon_r A}{d}$, C is inversely proportional to d, so as d decreases, C increases</p>	<p>Relationship Effect of water molecules on distance Link to capacitance</p>	1 1 1	3	3.7.4.2
06.3	 <p>When the humidity is zero, the capacitance is 282 μF, and when it is 100%, the capacitance is 330 mF, $C_{100} = \frac{\epsilon_0(\epsilon_r + \epsilon_w)A}{d}$ and $C_0 = \frac{\epsilon_0\epsilon_r A}{d}$ $\frac{C_{100}}{C_0} = \frac{\epsilon_0(\epsilon_r + \epsilon_w)}{d} \times \frac{d}{\epsilon_0\epsilon_r}$ $\frac{C_{100}}{C_0} = \frac{\epsilon_r + \epsilon_w}{\epsilon_r} = \frac{330}{285} = 1.17$</p>	<p>Graph starting at (0, 0), points plotted, linear line of best fit Correct labels/units</p> <p>Values between 280 μF and 285 mF acceptable</p> <p>Use of ratios of capacitances</p> <p>Method</p>	1 1 1 1	1 1	3.7.4.2

A Level AQA Physics

16 Capacitance – answers

Question	Answers	Extra information	Mark	AO	Spec reference
	$\epsilon_r + \epsilon_w = 1.17 \epsilon_r$ $\epsilon_w = 0.17 \epsilon_r$ $\epsilon_r = \frac{80}{0.17} = 471$				
06.4	$C_0 = \frac{\epsilon_0 \epsilon_r A}{d}$ $d = \frac{\epsilon_0 \epsilon_r A}{C_0}$ $= \frac{8.85 \times 10^{-12} \times 470 \times (10.8 \times 10^{-3} \times 3.81 \times 10^{-3})}{282 \times 10^{-12}}$ $= 1.7(1) \times 10^{-7} \text{ m which is about } 0.2 \times 10^{-6} \text{ m}$	<p>Use of equation</p> <p>Answer/comparison</p>	<p>1</p> <p>1</p>	2	
06.5	<p>Field strength (assuming parallel plates) = $\frac{V}{d}$</p> <p>So $V = \text{field strength} \times d = 74\,000 \times 1.7(1) \times 10^{-7} \text{ m} = 1.26 \times 10^{-2} \text{ V}$</p> $R = \frac{\rho l}{A} = \frac{10^{12} \times 1.7 \times 10^{-7}}{10.8 \times 10^{-3} \times 3.81 \times 10^3} = 4.13 \times 10^6 \Omega$ $I = \frac{V}{R} = \frac{1.26 \times 10^{-2} \text{ V}}{4.13 \times 10^6 \Omega} = 3.05 \times 10^{-12} \text{ A}$ <p>This is an extremely small current that would be very difficult to measure</p>	<p>Answer = $1.48 \times 10^{-2} \text{ V}$ if 0.2 mm used</p> <p>Answer</p> <p>Answer</p> <p>Comment</p>	<p>1</p> <p>1</p> <p>1</p> <p>1</p>	3	3.7.3.3 3.5.1.3
07.1	$C = \frac{\epsilon_0 \epsilon_r A}{d}, \epsilon_r = 1$ $= \frac{8.85 \times 10^{-12} \times 150 \times 10^{-4}}{0.1} = 1.33 \times 10^{-12} \text{ F}$ $Q = CV = 1.33 \times 10^{-12} \times 4000 = 5.31 \times 10^{-9} \text{ C}$	<p>Calculation of capacitance</p> <p>Charge</p>	<p>1</p> <p>1</p>	2	3.7.4.2
07.2	<p>When the ball touches the plate, electrons are transferred to it, giving the ball a net negative charge and it is attracted to the other plate/repelled from the negative plate</p> <p>When it touches the positive plate, the electrons are transferred to the plate, so it is repelled from the plate</p>	<p>Transfer of electrons used</p> <p>Correct attraction/repulsion</p>	<p>1</p> <p>1</p>	3	3.5.1.1

A Level AQA Physics

16 Capacitance – answers

Question	Answers	Extra information	Mark	AO	Spec reference
07.3	$T = 2\pi \sqrt{\frac{l}{g}}$ $T = 2\pi \sqrt{\frac{0.3}{9.8}} = 1.1 \text{ s}$ <p>So it would take about 0.5 s to travel between the plates</p>	Use of time period Answer	1 1	2	3.6.1.3
07.4	Current = $\frac{\text{charge}}{\text{time}} = \frac{0.1 \times 5.31 \times 10^{-9}}{0.5} = 1.1 \times 10^{-10} \text{ A}$	Answer	1	2	3.5.1.1
07.5	<p>The pd would decrease</p> $C = \frac{\epsilon_0 \epsilon_r A}{d}$ <p>And $Q = CV$ where Q is constant</p> $Q = \frac{V \epsilon_0 \epsilon_r A}{d}$ $Qd = V \epsilon_0 \epsilon_r A$ <p>p.d. is proportional to d</p>		1 1	3	3.7.4.2
08.1	The dielectric would break down/the capacitor will conduct		1	1	3.7.4.2
08.2	$V = V_0 e^{-\frac{t}{RC}}$ $C = \frac{t}{R(\ln V_0 - \ln V)}$ <p>$t = 7200 \text{ s}, V = 1.5 \text{ V},$ $V_0 = 3 \text{ V}; C = \frac{7200}{10000(\ln 3 - \ln 1.5)} = 1.0 \text{ F}$ $V_0 = 6 \text{ V}; C = \frac{7200}{10000(\ln 6 - \ln 1.5)} = 0.51 \text{ F}$ 3.3 F capacitor The operating pd for the 0.5 F and 1.3 F capacitor is only 3V</p>	Expression for C , explicit or implied Values of C for both initial p.d.s Conclusion with reason	1 1 1	2	3.7.4.4

A Level AQA Physics

16 Capacitance – answers

Question	Answers	Extra information	Mark	AO	Spec reference
08.3	$Q = It = 1400 \times 10^{-3} \times 3600 = 5040 \text{ C}$ $E = QV = 5040 \times 3 = 1.5 \times 10^3 \text{ J}$ $E = \frac{1}{2} CV^2 = 0.5 \times 0.5 \times 3^2 = 2.25 \text{ J}$ $E = \frac{1}{2} CV^2 = 0.5 \times 1.3 \times 3^2 = 5.85 \text{ J}$ The energy is much less than that stored in the battery by a factor of 500	Calculation of energy	1	2	3.5.1.1 3.7.4.3
		Calculations of energy	1		
		Comment	1		
08.4	The battery has an internal resistance, r , so if a current flows the p.d. will be reduced by a p.d. of Ir , $V = \varepsilon - Ir$ Current in circuit $I = \frac{\varepsilon}{R+r}$ Terminal p.d. = $V = \varepsilon - Ir$ $V = \varepsilon - \frac{\varepsilon}{R+r} r$ So $\frac{r}{R+r} = \frac{1}{2}$ R is equal to the internal resistance of the battery	Explanation involving internal resistance	1	3	3.5.1.6
		Use of equation	1		
		Answer	1		

Skills box answers

Question	Answer
1(a)	Graph will look similar to the one in the worked example column, with a negative gradient and an intercept on the y-axis at 2.33.
1(b)	Gradient of graph should be -0.02 . This is equal to $\frac{-1}{RC}$, so $RC = 50 \text{ s}$.
1(c)	Capacitance = $\frac{50}{R} = \frac{50}{(330 \times 10^3)} \Omega = 1.5 \times 10^{-4} \text{ F}$.
2	Electrolytic capacitors must be connected using the polarity marked on the capacitor. Otherwise the capacitor will overheat and be damaged.
3	The value for RC using this capacitor and resistor is 2.9 s, so the voltage will decay very quickly and be difficult to measure using a multimeter and stopclock. However, a data logger could be set to take 10 measurements per second and so could be used.