

# A Level OCR Physics

## Chapter 12 Electrical circuits

Question	Answers	Extra information	Mark	AO spec reference
1(a)	<p><b>Level 3 (5–6 marks)</b> Clear explanation of method with correct diagram, clear instructions on how to control temperature and light intensity <b>and</b> clear analysis. <i>There is a well-developed line of reasoning which is clear and logically structured. The information presented is relevant and substantiated.</i></p> <p><b>Level 2 (3–4 marks)</b> Some explanation of method with diagram and either some analysis or some control methods explained. <i>There is a line of reasoning presented with some structure. The information presented is in the most part relevant and supported by some evidence.</i></p> <p><b>Level 1 (1–2 marks)</b> Limited explanation and diagram <b>or</b> limited analysis. <i>The information is basic and communicated in an unstructured way. The information is supported by limited evidence and the relationship to the evidence may not be clear.</i></p> <p><b>0 marks</b> No response or no response worthy of credit.</p>	<p><b>Indicative scientific points may include:</b></p> <p>Method:</p> <ul style="list-style-type: none"> <li>Solar cell in series with ammeter and variable resistor</li> <li>Voltmeter in parallel with variable resistor (or solar cell)</li> <li>Change the resistance of the circuit using the variable resistance and record a series of voltage and current readings.</li> </ul> <p>Control light intensity</p> <ul style="list-style-type: none"> <li>Use of lamp with shielding round solar cell (black card).</li> <li>keep the lamp at a constant distance</li> </ul> <p>Control of temperature</p> <ul style="list-style-type: none"> <li>Turn light on for short periods when taking reading and leave to cool</li> <li>Place a clear container with water between the solar cell and light source.</li> </ul> <p>Analysis:</p> <ul style="list-style-type: none"> <li>Plot a graph of voltage against current</li> <li>The y intercept is the e.m.f</li> <li>the gradient is the internal resistance.</li> </ul>	6 max	4.3.2 1.1.1 4.3.2 AO3 × 3 AO2 × 3
(b)	<p>Any sensible suggestion</p> <p>The emf depends on the light intensity/temperature so they can only quote a value for average conditions</p>		1	4.3.2 AO3
(c)	recognising $\varepsilon = 8.2 \text{ V}$		1	4.3.2

# A Level OCR Physics

## Chapter 12 Electrical circuits

Question	Answers	Extra information	Mark	AO spec reference
	Use of $\varepsilon = V + Ir$ $8.2 = 5.5 + (0.1 \times r)$ $2.7 = 0.1r$ $r = 27 \Omega$		1	AO2
<b>(d)(i)</b>	Series: $\varepsilon = 2.5 \text{ V} + 2.5 \text{ V} = 5.0 \text{ V}$ $r = 4 \Omega + 4 \Omega = 8 \Omega$	1 mark for both correct	1	4.3.1 AO2
<b>(ii)</b>	Parallel: $\varepsilon = 2.5 \text{ V}$ $r = (1/4 + 1/4)^{-1} = 2 \Omega$		1	4.3.1 AO2
<b>2(a)</b>	The sum of the p.d. is equal to the sum of the emfs in a closed loop.		1	4.3.1 AO1
<b>(b)</b>	$V = IR$ $V = 0.15 \times 40 = 6 \text{ V}$		1	4.2.3 AO1
<b>(c)</b>	p.d. = $9 - (6 + 2) = 1 \text{ V}$ $V = IR$ $I = V/R = 1 / 2.5 = 0.4 \text{ A}$	ECF	1 1	4.3.1 4.2.3 AO2
<b>(d)</b>	Current through A = $0.4 - 0.15 = 0.25 \text{ A}$ p.d. across A = $6 - (10 \times 0.25) = 6 - 2.5 = 3.5 \text{ V}$ $R = 3.5/0.25 = 14 \Omega$		1 1 1	4.3.1 AO2
<b>(e)</b>	$R = V/I = 2/0.4 = 5 \Omega$		1 1	4.3.1 AO2
<b>3(a)</b>	1 litre = $1000 \text{ cm}^3$ 191 litres per hour = $53 \text{ cm}^3 \text{ s}^{-1}$		1 1	3.2.4 AO2

# A Level OCR Physics

## Chapter 12 Electrical circuits

Question	Answers	Extra information	Mark	AO spec reference
	mass per second = $\rho V = 1000 \times 53 \times 10^{-6} = 0.053 \text{ kg s}^{-1}$			
(b)	$P = \Delta W / \Delta t$ or $gpe = mgh$ $p = 0.053 \times 9.81 \times 0.3 = 0.16 \text{ W}$		1 1	3.3.2 AO2
(c)	$P = VI$ $I = 1.2/5 = 0.24 \text{ A}$		1	4.2.5 AO1
(d)	Use of $\varepsilon = I(R + r)$ $\varepsilon = iR + Ir = V + Ir$ $6 = 5 + (0.24 \times r)$ $1 = 0.24r$ $r = 4.2 \Omega$ OR Calc resistance of pump $R = V/I = 5/0.24 = 20.8 \Omega$ $\varepsilon = I(R + r)$ $6 = 0.24(20.8 + r)$ $6 = 5 + 0.24r$		1  1 1	4.3.2 AO2
4(a)	$P = VI$ A $I = 0.7/3.5 = 0.2 \text{ A}$ B $I = 1.95/6.5 = 0.3 \text{ A}$ C $I = 0.3 / 1.5 = 0.2 \text{ A}$	2 marks max for all three correct.	1 1	4.2.5 AO1
(b)	$I = 0.2 \text{ A} + 0.3 \text{ A} + 0.2 \text{ A} = 0.7 \text{ A}$		1	4.1.1 AO2
(c)	p.d. across $R_1 = 9.0 - 6.5 = 2.5 \text{ V}$ $R_1 = V/I = 2.5/0.7 = 3.6 \Omega$	allow ecf from answer to 4(b)	1 1	4.3.1 4.2.3 AO2

# A Level OCR Physics

## Chapter 12 Electrical circuits

Question	Answers	Extra information	Mark	AO spec reference
(d)	p.d. across $R_3 = 6.5 - 1.5 = 5.0 \text{ V}$ $R_3 = V/I = 5.0/0.2 = 25 \Omega$		1 1	4.3.1 4.2.3 AO2
5(a)	In series: $\varepsilon = 1.5 \text{ V} + 1.5 \text{ V} = 3.0 \text{ V}$ $r = 0.5 \Omega + 0.5 \Omega = 1.0 \Omega$		1 1	4.3.1 AO1
(b)	In parallel: $\varepsilon = 1.5 \text{ V}$ $r = (1/0.5 + 1/0.5)^{-1} = 0.25 \Omega$		1 1	4.3.1 AO1
(c)	2 cells in parallel with one cell in series		1	4.3.1 AO2
(d)	Use of $\varepsilon = V + Ir$ or $r = \frac{3}{4} = 0.75 \Omega$ $3.0 = I(2.0 + 0.75)$ $I = 1.1 \text{ A}$	ECF	1 1	4.3.2 AO2
(e)	$P = I^2R = 1.1^2 \times 2 = 2.4 \text{ W}$	ECF	1	4.2.5 AO2
6(a)	Diagram showing 3 resistors connected in series		1	4.3.1 AO1
(b)	Total resistance = $33 \Omega + 110 \Omega + 67 \Omega = 210 \Omega$		1	4.3.1 AO1
(c)	Diagram showing three resistors connected in parallel		1	4.3.1 AO1
(d)	Total resistance = $1/(1/110 + 1/67 + 1/33)$ $R = 18 \Omega$		1 1	4.3.1 AO2

# A Level OCR Physics

## Chapter 12 Electrical circuits

Question	Answers	Extra information	Mark	AO spec reference
(e)	Diagram showing two $33\ \Omega$ resistors in series and also in parallel with two other $33\ \Omega$ resistors in series		1	4.3.1 AO2
(f)	Accept any sensible suggestion: Smaller current through each resistor / less power transferred by each resistor / still resistance if 1 resistor breaks		1	4.3.1 AO3
7(a)	As temperature increases resistance of thermistor decreases pd across thermistor decreases or pd across fixed resistor R increases $V_{OUT}$ increases which means it will switch something on when the temperature increases.		1  1	4.2.4 4.3.3 AO2
(b)	The resistance decreases non-linearly with temperature. This is because the number of charge carriers increase in the thermistor.		1 1	4.2.4 AO2
(c)	$60\ ^\circ\text{C}$ $280\ \Omega$ allow $\pm 5\ \Omega$ $100\ ^\circ\text{C}$ $190\ \Omega$ allow $\pm 5\ \Omega$	Both correct for mark	1	1.1.3 AO1
(d)	Variable resistor needed Range: $R/5 = 280/4$ $R = 350\ \Omega$ $R/5 = 190/4$ $R = 238\ \Omega$	mark for either calculation of value	1 1	4.3.3 AO2
8(a)	LDR and resistor drawn in series correct symbols Some indication that $V_{OUT}$ is across the fixed resistor		1 1	4.3.3 4.2.3 AO2
(b)	The resistance of the LDR decreases so current increases The pd across the fixed resistor increases since current increases $V = IR$ has a greater share of the total resistance so pd increases	This first mark maybe given even if $V_{OUT}$ wrongly labelled in 8(a)	1  1	4.3.3 4.2.3 AO2

# A Level OCR Physics

## Chapter 12 Electrical circuits

Question	Answers	Extra information	Mark	AO spec reference
(c)	<p>Examples of calculation:</p> <p>1 M<math>\Omega</math> Dark <math>V_{OUT} = (1M/2M) \times 6 = 3 \text{ V}</math> Light <math>V_{OUT} = (1 \times 10^6 / (1 \times 10^6 + 5400)) \times 6 = 6 \text{ V}</math></p> <p>10 k<math>\Omega</math>: Dark <math>V_{OUT} = (1 \times 10^4 / (1 \times 10^4 + 1 \times 10^6)) \times 6 = 0.06 \text{ V}</math> Light <math>V_{OUT} = (1 \times 10^4 / (1 \times 10^4 + 5400)) \times 6 = 4 \text{ V}</math></p> <p>1 k<math>\Omega</math>: Dark <math>V_{OUT} = (1 \times 10^3 / (1 \times 10^3 + 1 \times 10^6)) \times 6 = 0.006 \text{ V}</math> Light <math>V_{OUT} = (1 \times 10^3 / (1 \times 10^3 + 5400)) \times 6 = 0.9 \text{ V}</math></p> <p>10 k<math>\Omega</math> has the greatest range</p>	<p>Examples of calculations max 3 1 mark for correct deduction with explanation</p>	Max 4	<p>4.3.3 AO2 <math>\times</math> 2 AO3 <math>\times</math> 2</p>